

Chapter 8


Digital and Analog Interfacing Methods

Lesson 11 Part a

Analog Input and Temperature and pressure measuring Interfaces

Vdc or a.c. from
an oscillator

Whetstone Bridge

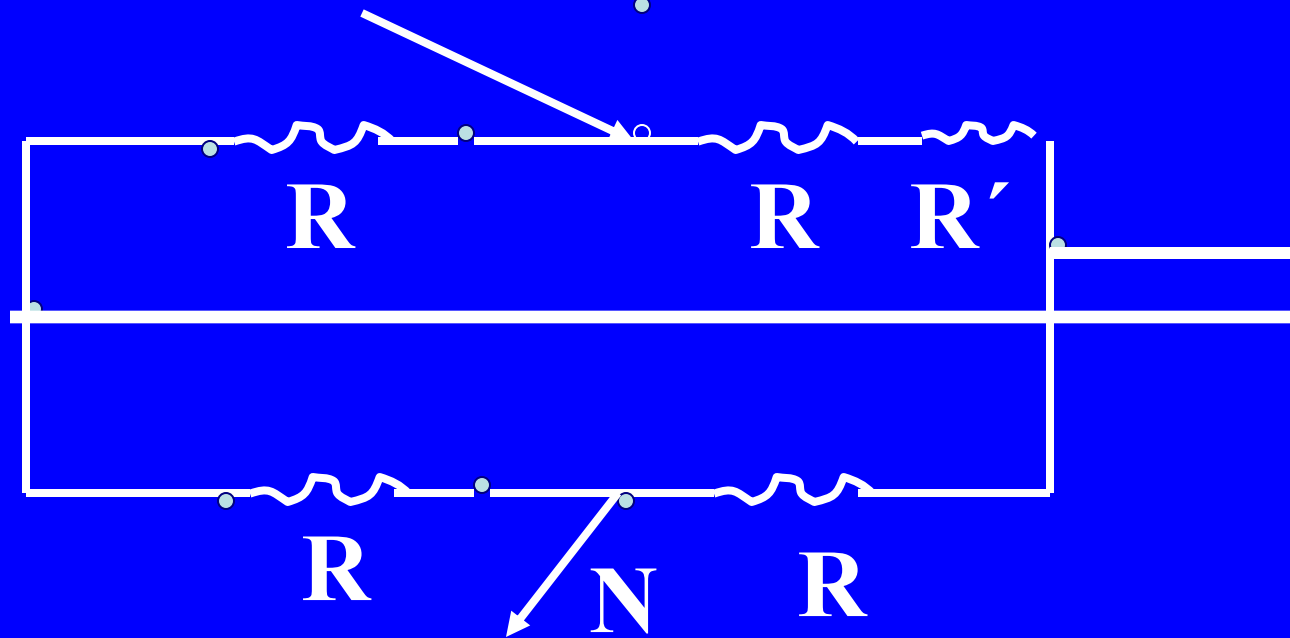

Wheatstone Bridge


- All four arms Resistances equal when $R' = 0$, bridge is balanced
- Output = 0V for any analog input when bridge is balanced

Whetstone Bridge

- Assume R' is resistance of the sensor of a physical quantity.
- All but one Resistance is equal, the output depends on the ratio of $(R + R')/R$, bridge is not balanced
- Output not = 0V for a non-zero analog input when bridge is not balanced
- All Resistances are of the same order, bridge gives maximum sensitivity

RTD (Resistance change on Temperature Detector) senses temperature by resistance changes
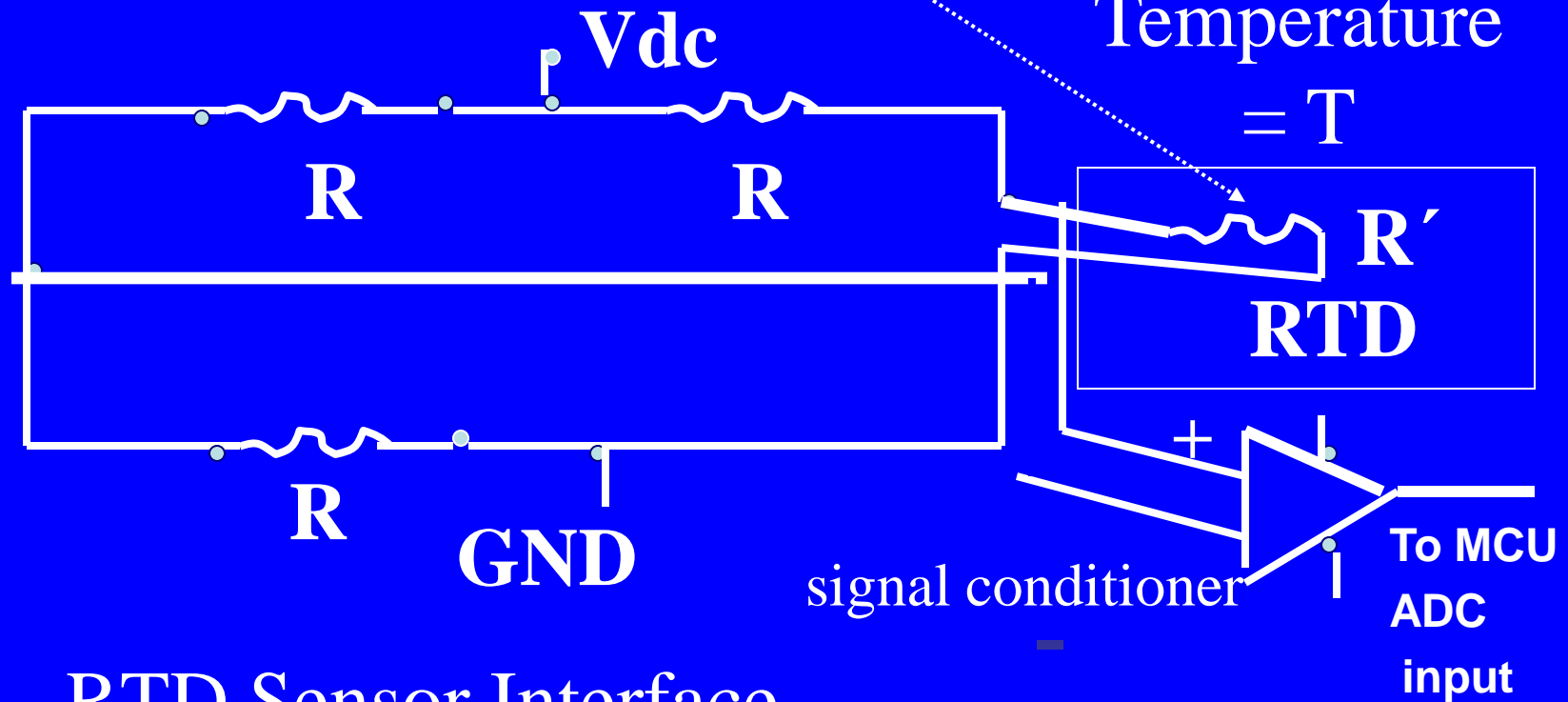
$$R' = R_0[1 + \alpha_T T + \beta_T T^2]$$
$$\text{or } R' = R_0[1 - \alpha_T T - \beta_T T^2]$$




RTD Sensor Interface

Bismuth Resistance change on Pressure

Senses Pressure by resistance changes

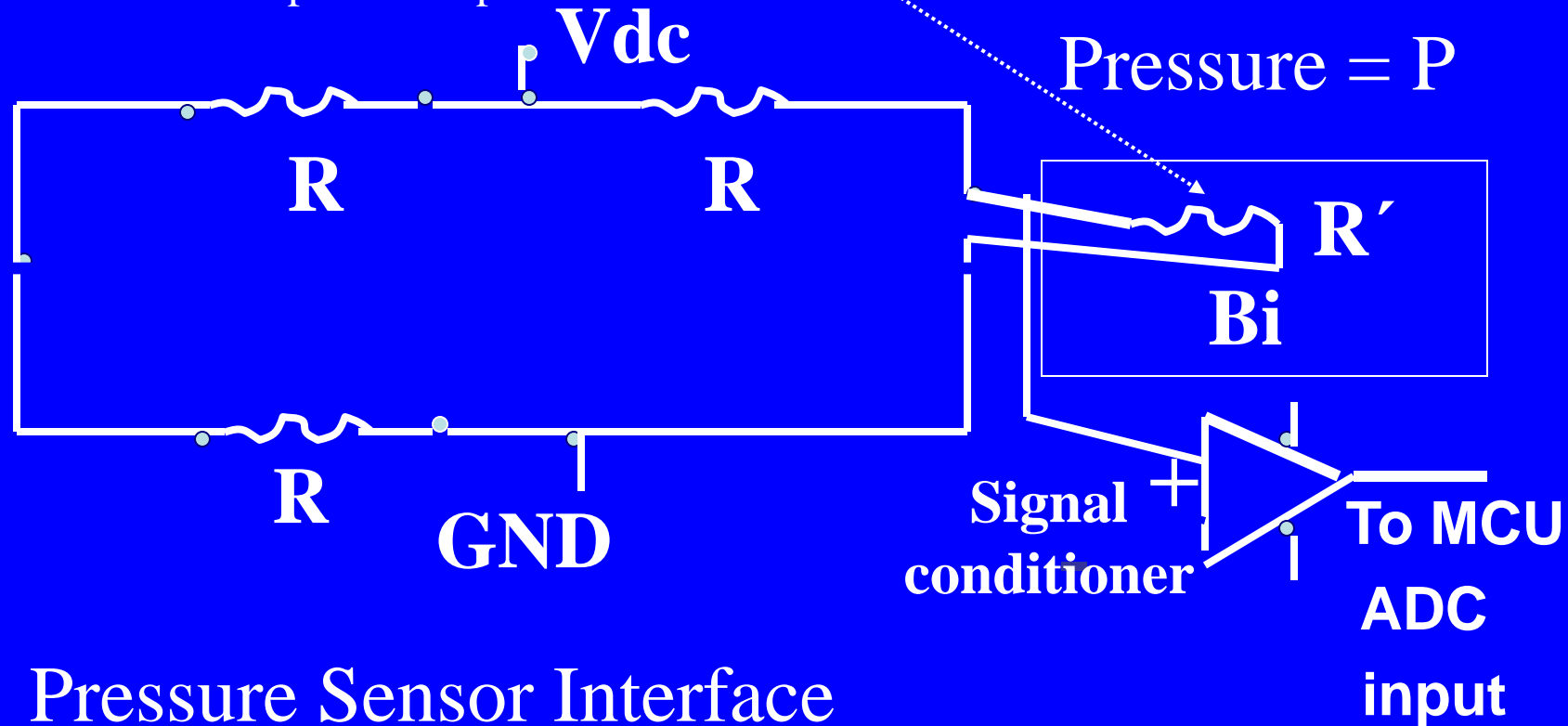
$$P' = P_0 [1 + \alpha_p P + \beta_p P^2]$$
$$\text{or } P' = P_0 [1 - \alpha_p P - \beta_p P^2]$$




Pressure Sensor Interface

Signal Conditioner

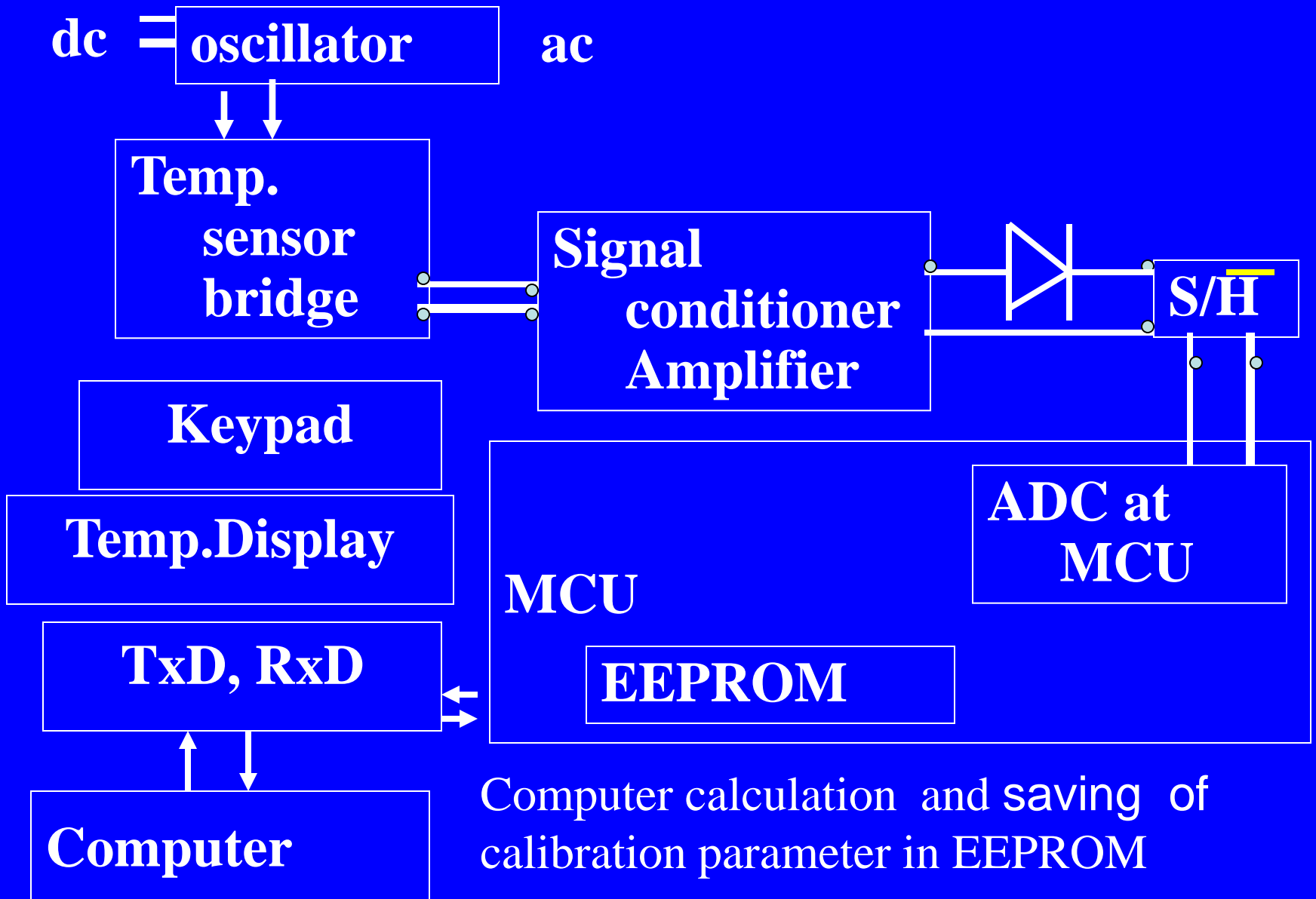- Design such that output obtained = 0 V for input to ADC when temperature or pressure is at certain minimum limiting value and ADC output is 00000000.
- For obtaining reference Voltage input V_{ref} to ADC when temperature or pressure is at certain maximum limiting value and ADC output is 11111111.



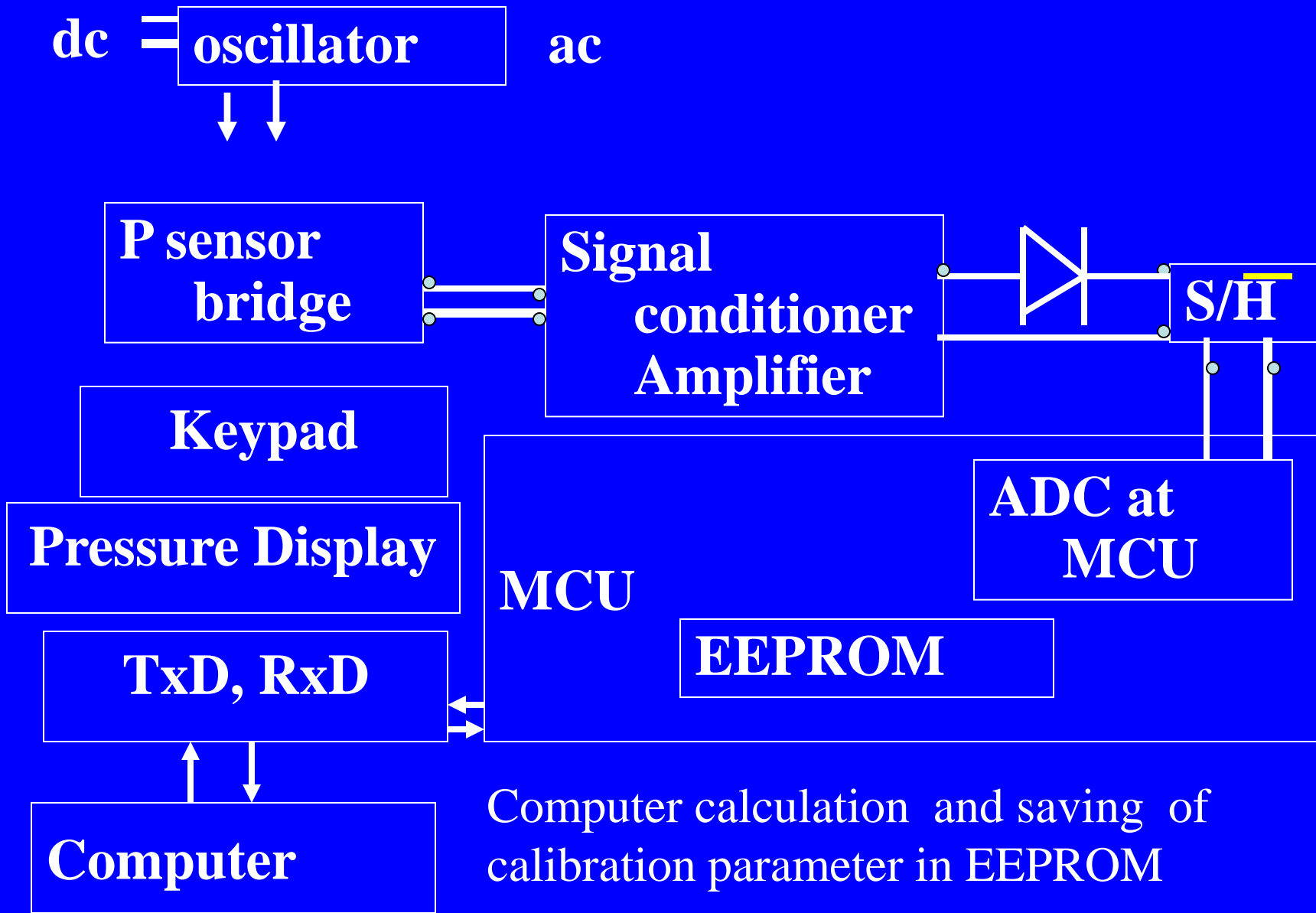

TxD and RxD Interface to Computer

- Keypad for entering the sample name, physical parameter name, time and date of measurements and other features
- Computer calculation of calibration parameters α_T and β_T , α_p and β_p and saving in EEPROM
- Periodic calculation and revision of calibration parameters and saving in EEPROM (if required)

TxD and RxD Interface to Computer

- Computer records permanently the readings at different instances
- Computer graphical presentations for parameter as a function of time

Summary

We learnt

Analog Inputs from sensors

- Whetstone bridge
- Signal conditioning amplifier and S/H circuit
- MCU ADC input

End of Lesson 11 Part a

Analog Input and Temperature and pressure measuring Interfaces