

Chapter 8

Digital and Analog Interfacing Methods

Lesson 11 Part 6

Interface for generating Analog Outputs for dc motor and speed and direction control using Pulse Width Modulation

Pulse width modulation

1. A Pulse width modulated output obtained using a digital number x .
2. A analog output is obtained by integrating the Pulse width modulated pulses.
3. Pulse frequency is proportional to clock input frequency to a n -bit pulse accumulator
4. Pulse-width of modulated pulse is proportional to value $(2^{n-1} - x)$ when x is loaded into a modulation register.

Pulse width modulation


5. The analog output is proportional to $\pm(0.5 - x)$ where value x loads into PWM register.
6. The number x generates output as if it is obtained by a DAC function.
7. Modulation % = ± 0.5 of Period for pulse width is '1' divided by Total period of pulse at 1 and at 0 multiplied by 100.

PWM output

- x = digital number in an n -bit PWM register
- PWM output bit = 1 for period $T1$
- PWM output bit = 0 for period $T2$
- $T1 \propto \underline{(2^{n-1} - x)}$;
- $T2 \propto (x)$;
- $(T1 + T2) \propto (2^{n-1})$, where
- V Output of integrator $\propto k \cdot (T1) / (T1 + T2)$
- k is integration constant

8-bit PWM example

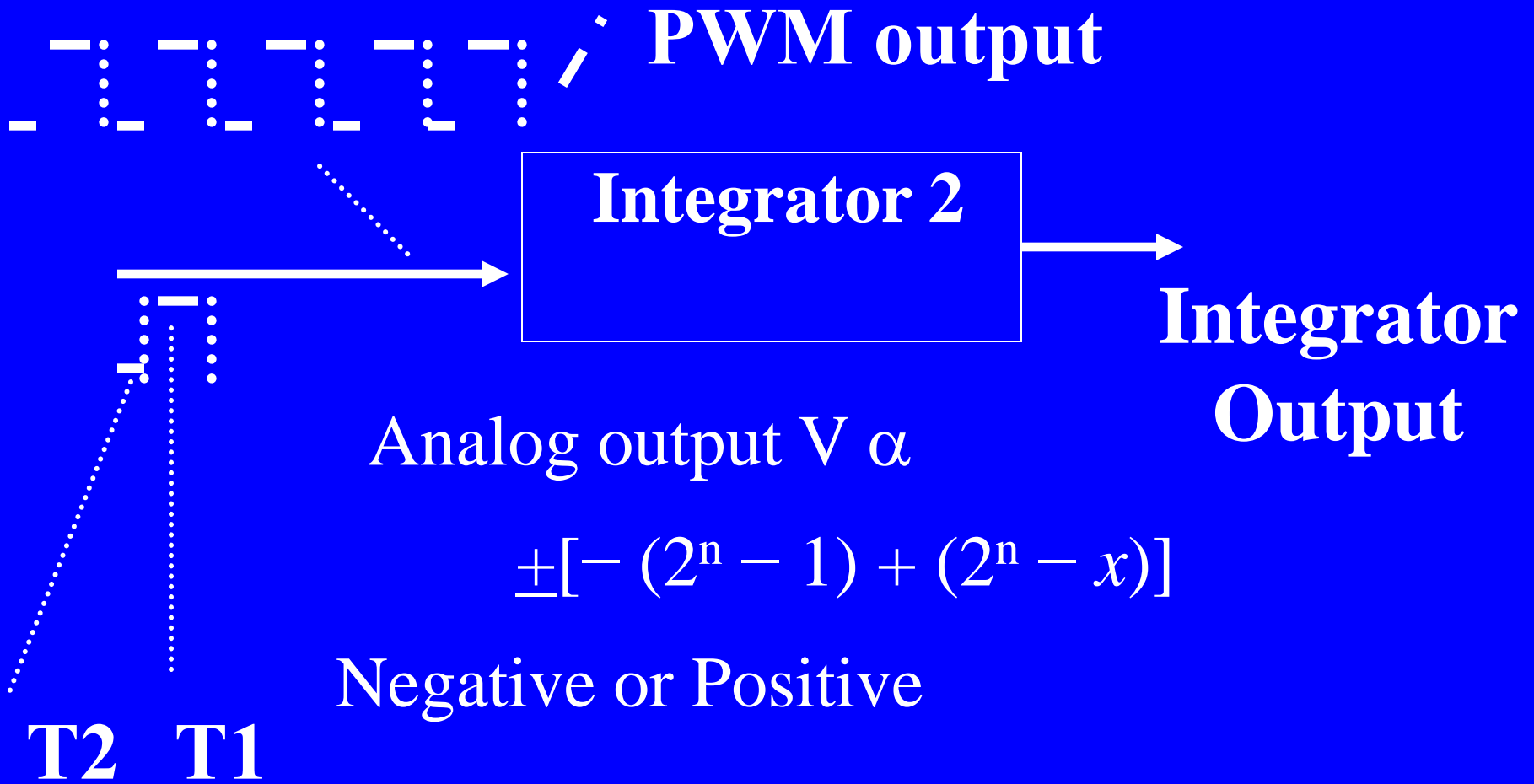
- When x in PWM register = all 0s = 00000000 (=0d). Let pulse-width $T1 = 0$ ms, and $T1+T2 = 128 \times 5 \mu\text{s} = 0.64$ ms
- $x = 01000000$ (= 64d) generate output width $T1 = 0.32$ ms, when register count-input pulse periods equal $(0.32/64)$ ms = 5 μs
- $x = 11111111$ (= 255d) generate width $T1 = 0.6325$ ms.



Analog Outputs Interfaces

- PWM plus Integrator
- PWM and inverse of PWM output to integrator-2 for d.c.motor speed and direction control
- Speed controls by $\pm(2^{n-1} - x)$
- On-Off control by two NAND gates second input
- Direction controls by $x > 2^{n-1}$ or $x < 2^{n-1}$

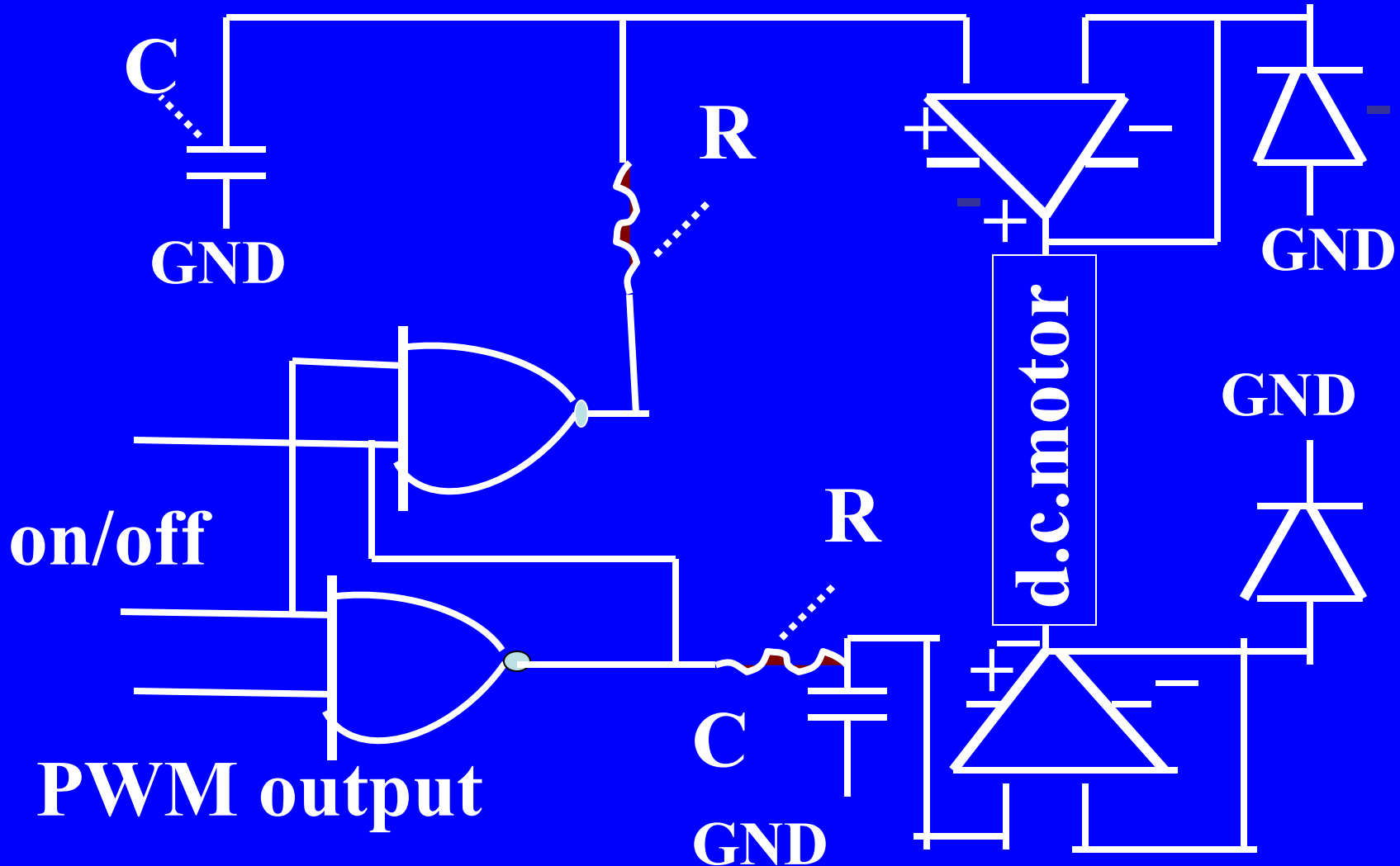Integrator PWM output for current, speed and direction control of d. c. motor



Summary

We learnt

- Analog Outputs is obtained after integration of pulse width modulated output
- Pulse width of the modulated pulses is proportional to value loaded in pulse width modulation register
- Pulse frequency is proportional to clock input frequency to pulse accumulator
- Integrator can be designed such that + or – or both – and \pm analog outputs obtained as a function of x between $\pm(2^{n-1} - x)$

End of Lesson 11 Part e

Interface for generating Analog Outputs for dc motor and speed and direction control using Pulse Width Modulation