

# Chapter 08: The Memory System

## Lesson 05:

### **SRAM and DRAM Memory chips and their internal Organisation**

# Objective


- Understand the process of read, write into bit cells
- Learn Semiconductor Main Memories - SRAM and DRAM

# Memory Chip Organisation

# Memory Chip

- Same basic structure in SRAM and DRAM memory chips
- Data stored in a rectangular array of bit cells
- Each cell holds 1 bit of data

# Memory chip organisation

 

# MUX (multiplexer) during read

- A circuit which at an instance selects from the number of inputs and gives one of the input in the output (for example, during read)
- Which one that depends on input-address or channel selected for the output

# MUX Logic during write

- A MUX (multiplexer) function as demultiplexer logic circuit (for example, during write), when at an instance it selects one line from the number of output lines and gives its input at the line

# Decoder Logic

- A logic circuit, which at an instance activates one of the output line, which it selects as per the input-address lines

# Accesses of bit cells in memory

# Read Operation

- Half of the address bits to be read (generally the high-order bits) is fed into a decoder
- The decoder asserts (drives high) a word line corresponding to the value of its input bits
- Causes all of the bit cells in the corresponding row to drive their values onto the bit lines that they are connected to

# Read Operation

- The other half of the address bits (generally the low-order bits) is then used as the addressed bit-select input to a multiplexer that selects the appropriate bit line and drives its output onto the output pins of the chip

# Write (store) Operation

- To store data on the chip, the same process is used as for the read, except the value to be written is driven on the appropriate bit line and written into the selected bit cell

# Number of Output Bits on Access

- Most memory chips generate more than 1 bit of output
- This is done either by building several arrays of bit cells, each of which produces one bit of output, or by designing a multiplexer that selects the outputs of several of the bit lines and drives them on the chip's outputs

# Speed of a Memory Chip Access

- Determined by a number of factors, including the length of the bit and word lines and how the bit cells are constructed
- Longer bit and word lines have higher capacitances and resistances, so it takes longer to drive a signal on these wires as their lengths increase

# Modern memory chips

- To lower the capacitances and resistances to reduce the access latency— constructed out of many small arrays of bit cells to keep the word and bit lines short

# Effect of Techniques used in constructing the bit cells

- Speed of the memory chip— because they affect how much current is available to drive the output of the bit cell onto the bit lines
- The current determines how long it takes to propagate the bit cell's output to the multiplexer
- SRAM bit cells drive much more current than DRAM bit cells
- SRAMs tend to be much faster than DRAMs

# SRAMs and DRAMs

# SRAMs typically much faster than DRAMs

- In SRAMs, an active device (the inverter) drives the value stored in the bit cell onto the bit line and inverted bit line


# DRAMs typically slower than SRAMs

- In DRAMs, the capacitor is connected to the bit line when the word line is asserted, which is a much weaker signal than the one produced by the inverters in an SRAM bit cell
- Thus, it takes much longer for the output of a DRAM bit cell to be driven onto its bit line than it takes for an SRAM bit cell to drive an equivalent bit line

# Main difference between SRAMs and DRAMs

- Bit cells construction
- Core of an SRAM bit cell consists of two inverters connected in a back-to-back configuration
- Core of an DRAM bit consists of a transistor and capacitor


# Core of an SRAM bit cell

 

# SRAM

- Once a value has been placed in the bit cell, the ring structure of the two inverters will maintain the value indefinitely because each inverter's input is the opposite of the other's
- This is the reason why SRAMs function as the static RAMs; the values stored in the RAM remain there as long as power is applied to the device

# Core of a DRAM bit cell

 

# DRAMs

- Loses their stored values over time, which is why they are known as *dynamic* RAMs

# SRAM smaller capacities than DRAMs much larger capacities

- Assume SRAMs constructed in the same fabrication technology
- SRAMs require many more devices to implement a bit cell
- Each inverter typically requires two transistors, for a total of six transistors in the bit cell
- In contrast, a DRAM bit cell requires only one transistor and one capacitor, which take up much less space on the chip

# Reading from SRAM


- To read a value from the bit cell, the word line driven high
- Two transistors connects the outputs of the inverters to the bit line and inverted bit line
- These signals can then be read by the multiplexer and sent to the output of the chip

# Writing into SRAM


- Writing an SRAM bit cell is accomplished by asserting the word line and driving the appropriate values on the bit line and inverted bit line
- As long as the device driving the bit line is stronger than the inverter, the values on the bit line will dominate the value originally stored in the bit cell, and will be stored in the bit cell when the word line is de-asserted

# Memory chip

# 8 MB RAM

 

# 64 MB RAM

 


# Bus signals to a Memory chip


# Bus Signals

- $t_0$  to  $t_2$  CS enable and  $t_0 + \Delta t_0$  to  $t_0 + \Delta t_0 + \Delta t_0'$  Address Latch enable
- $t_0 + \Delta t_0 + \Delta t_0' + \Delta t_0''$  to  $t_2 - \Delta t_2'$  RD enable
- $t_0 + \Delta t_0 + \Delta t_0' + \Delta t_0''$  to  $t_2 - \Delta t_2'$  ~~WR~~ enable
- $t_0 + \Delta t_0 + \Delta t_0''$  to  $t_2 + \Delta t_2''$  Address Lines
- $t_0 + \Delta t_0 + \Delta t_0' + \Delta t_0'' + \Delta t_0'''$  to  $t_2 - \Delta t_2''$  Read at Data Lines
- $t_0 + \Delta t_0 + \Delta t_0' + \Delta t_0'' + \Delta t_0'''$  to  $t_2 - \Delta t_2' + \Delta t_2'''$  Write at Data Lines

# $2^{22} \times 8$ SRAM

 

# Read and write

 

# Summary

# We learnt

- Understand the process of read, write into bit cells
- Semiconductor Main Memories - SRAM and DRAMs
- Bit cell in SRAM
- Bit cell in DRAM
- Chip signals
- Bus signals

End of Lesson 05 on  
**SRAM and DRAM Memory chips and their  
internal Organisation**