

Chapter 8

Digital and Analog Interfacing Methods

Lesson 11 Part d

Interface for generating Analog Outputs using Pulse Width Modulation

Pulse width modulation

1. A Pulse width modulated output obtained using a digital number x .
2. A analog output is obtained by integrating the Pulse width modulated pulses.
3. Pulse frequency is proportional to clock input frequency to a n -bit pulse accumulator
4. Pulse-width of modulated pulse is proportional to value $(2^n - x)$ when x is loaded into a modulation register.

Pulse width modulation

5. The analog output is proportional to value x loaded into PWM register.
6. The number x generates output as if it is obtained by a DAC function.
7. Modulation % = $\frac{\text{Period for pulse width is '1'}}{\text{Total period of pulse at 1 and at 0}} \times 100$.


PWM output


- x = digital number in an n -bit PWM register
- PWM output bit = 1 for period $T1$
- PWM output bit = 0 for period $T2$
- $T1 \propto (2^n - x)$;
- $T2 \propto (x)$;
- $(T1 + T2) \propto (2^n)$, where
- V Output of integrator $\propto k \cdot (T1) / (T1 + T2)$
- k is integration constant

8-bit PWM example

- When x in PWM register = all 0s = 00000000 (=0d). Let pulse-width $T1 = 0$ ms, and $T1+T2 = 256 \times 5 \mu\text{s} = 1.28$ ms
- $x = 10000000$ (= 128d) generate output width $T1 = 0.64$ ms, when register count-input pulse periods equal $(0.64/128)$ ms = $5 \mu\text{s}$
- $x = 11111111$ (= 255d) generate width $T1 = 1.275$ ms.


n-bit PWM example

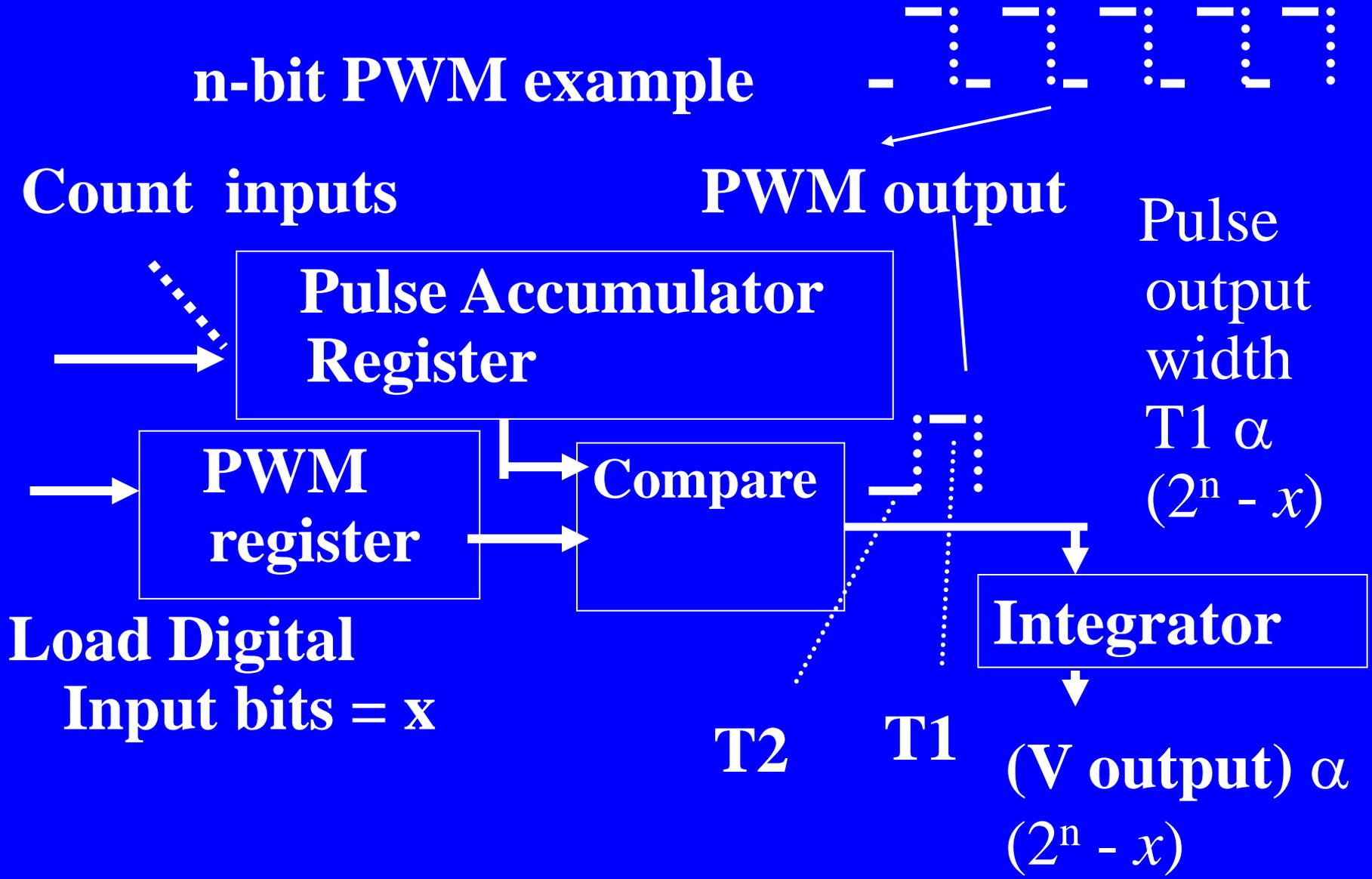


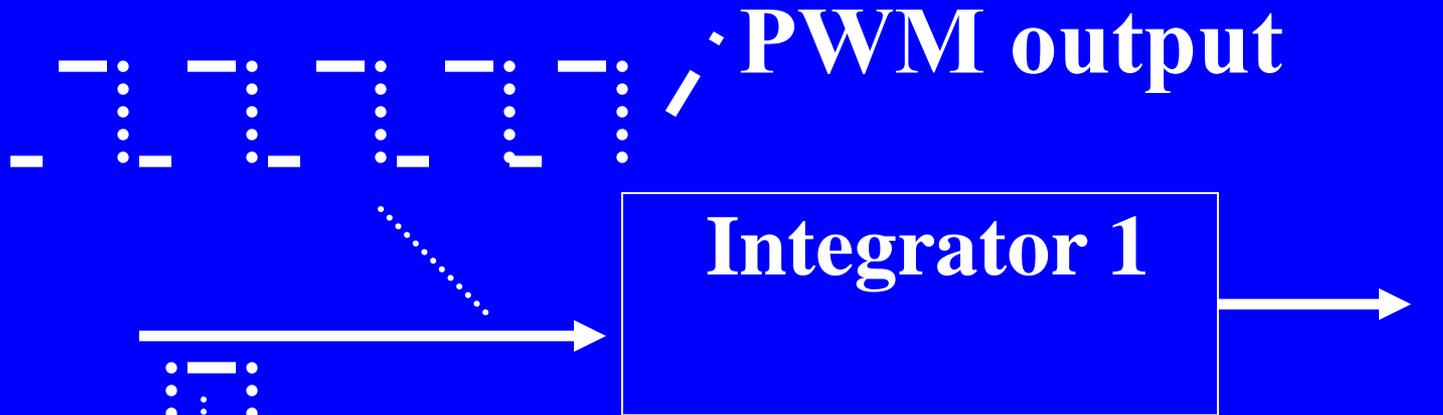


Analog output $V \alpha + (2^n - x)$

Integrator Output

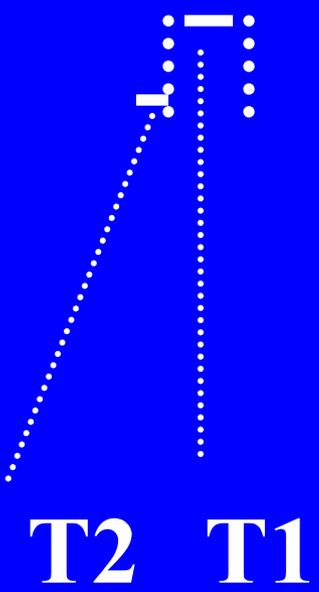


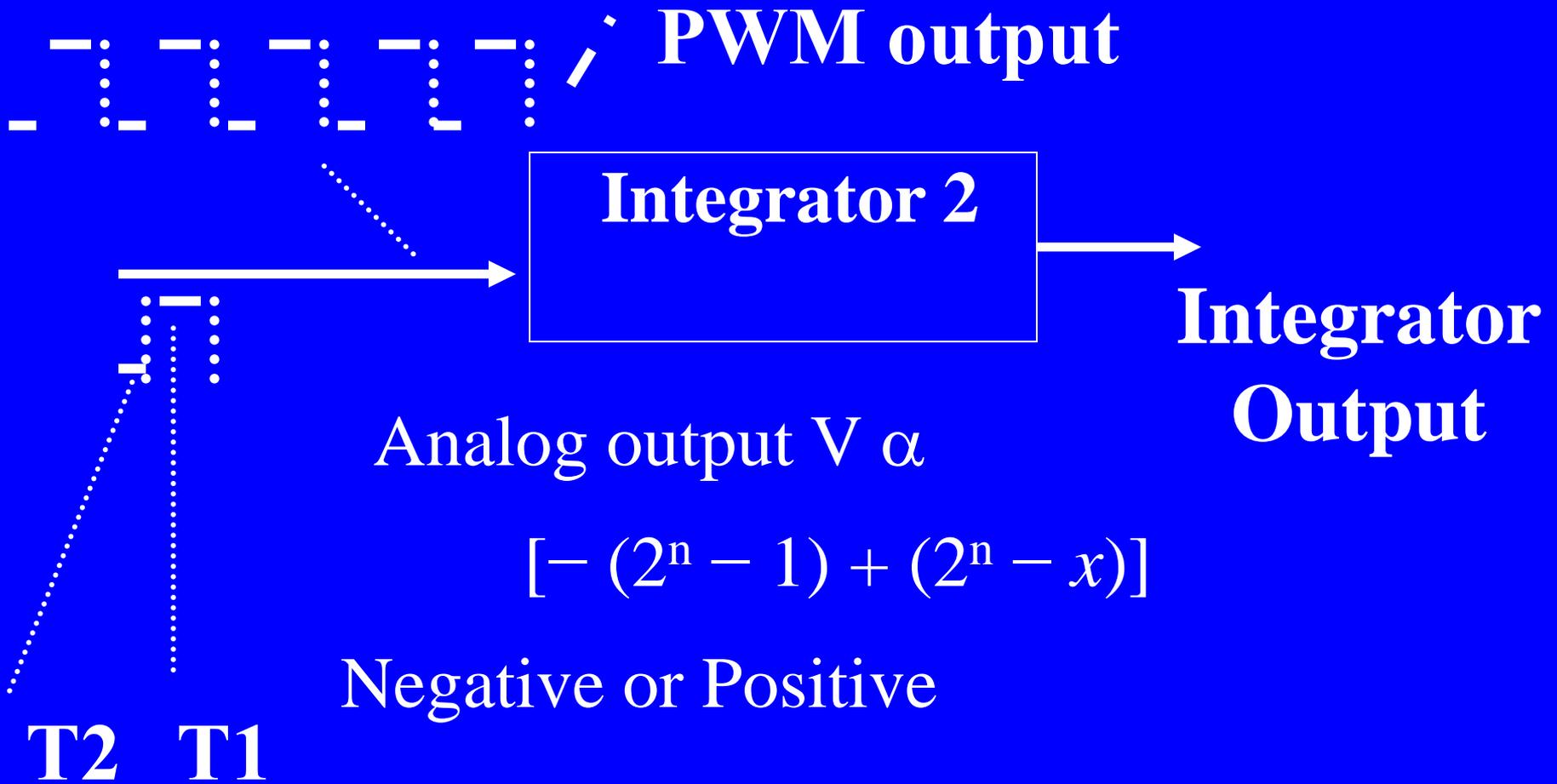

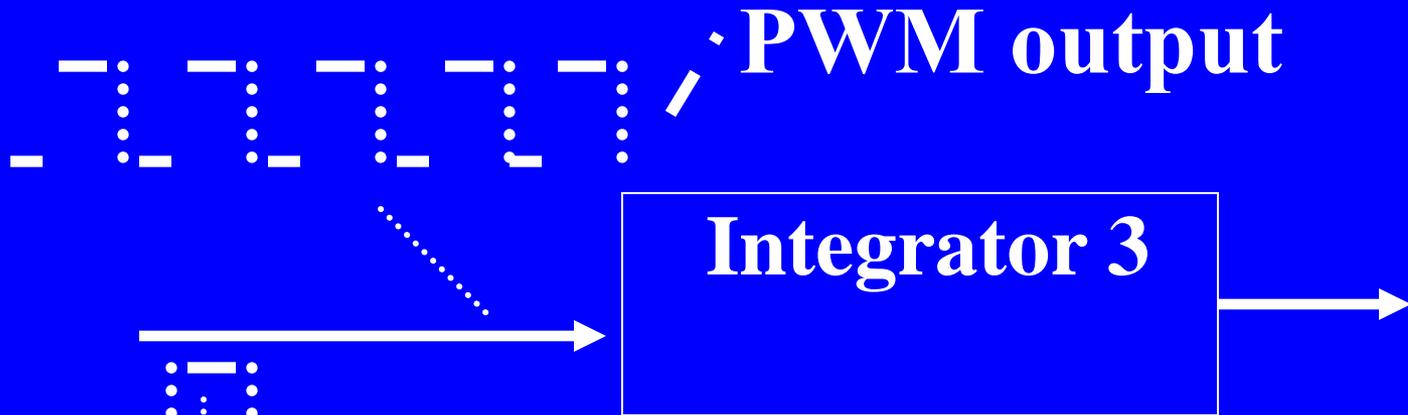

Analog output $V \propto [-(2^n - x)]$

Integrator Output

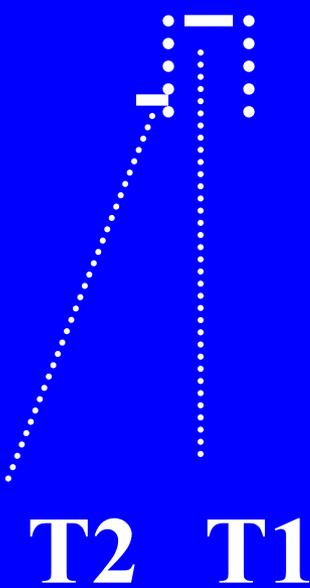

Summary

We learnt

- Analog Outputs is obtained after integration of pulse width modulated output
- Pulse width of the modulated pulses is proportional to value loaded in pulse width modulation register
- Pulse frequency is proportional to clock input frequency to pulse accumulator
- Integrator can be designed such that + or – or both – and $\frac{+}{-}$ analog outputs obtained as a function of x between 0% and 100%.

End of Lesson 11 Part d

Interface for generating Analog Outputs